


Digital Circuit Fall 2019

Yuxuan Zhang, XJTU, 2160909016

Session 6 - Pulse generating and shaping

Session 6 Homework

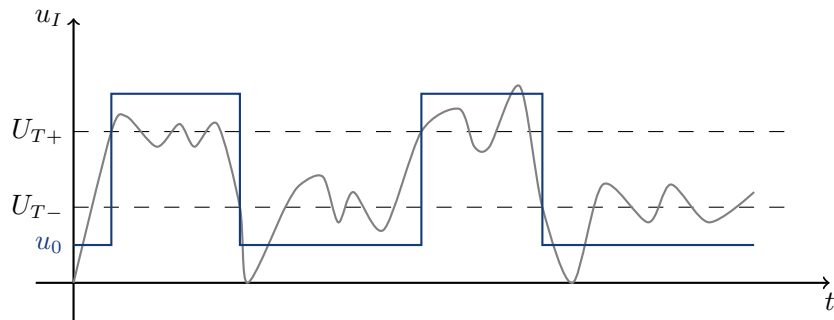- **Problem 1 - 9.1** Give the waveform of u_0 .



- **Problem 2 - 9.5** Given a 74121 connected as shown.

1. Calculate the range of delay time

$$CR \leq t_d \leq C(R + R_W)$$

$$3.57ms \leq t_d \leq 18.97ms$$

2. What's the functionality of the resistor next to R_w ?

It prevents short circuit when R_w is set to 0.

- **Problem 3 - 9.8**

1. Analyze the status of circuit when S is open.

When S remains open,

$$\overline{TR} \equiv V_{cc} > \frac{1}{3}V_{cc}$$

TH will be flipped to Low if it was High, and remains Low as a stable status.

Hence, u_0 holds on 0. The circuit is stable.

2. Let $C = 10 \mu F$, give the value of R so as the circuit outputs a pulse of $t_w = 10s$ when S is pressed.

Since the given design is a standard monostable trigger, we can use $t_w = RC \ln 3 = 10s$.

Hence, $R = 910 k\Omega$.

3. What's the value of R if $C = 0.1 \mu F$, $t_w = 5ms$? What value of t_w do we expect if we replace C by $1 \mu F$ with

the same R ?

$$t_w = RC \ln 3 = 5 \text{ ms}$$

$$R = \frac{5 \text{ ms}}{0.1 \mu\text{F} \cdot \ln 3} = 45.5 \text{ k}\Omega$$

$$\text{Replace} \Rightarrow C = 1 \mu\text{F}$$

$$t_w = 50 \text{ ms}$$

• **Problem 4 - 9.13 .**

1. What kind of function dose each of the 555 chip serve?

Each of them is a multivibrator.

2. Analyze the status of circuit when S is set to 1.

Charging time:

$$(\text{Chip1}) T_1 = (R_1 + R_2)C \ln 2 = 2.84 \text{ ms}$$

$$(\text{Chip2}) T_1 = (R_1 + R_2)C \ln 2 = 0.284 \text{ ms}$$

Discharge time:

$$(\text{Chip1}) T_2 = R_2 C \ln 2 = 1.53 \text{ ms}$$

$$(\text{Chip2}) T_2 = R_2 C \ln 2 = 0.153 \text{ ms}$$


Duty cycle:

$$(\text{Chip1}) F = 228.3 \text{ Hz}$$

$$(\text{Chip2}) F = 2.283 \text{ kHz}$$

Ratio 65%

3. Draw the wave form of both u_0 and u_1 when S is set to 2.

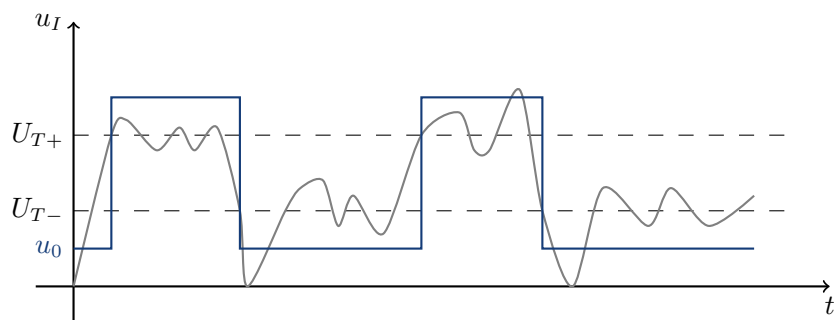

Session 7 - D/A and A/D converter

Session 7 Homework

- Problem 1 - 10.2 .
- Problem 2 - 10.6 .
- Problem 3 - 11.3 .
- Problem 4 - 11.12 .