

# Digital Circuit Fall 2019


Yuxuan Zhang, XJTU, 2160909016

## Session 6 - Pulse generating and shaping

---

### Session 1 Homework

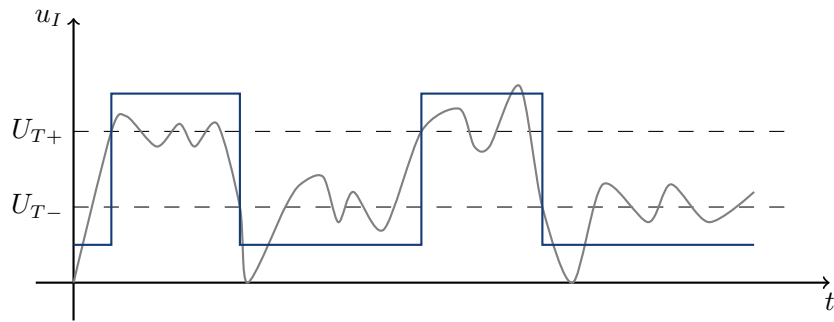- **Problem 1 - 9.1** Give the waveform of  $u_0$ .



- **Problem 2 - 9.5** Given a 74121 connected as shown.

1. Calculate the range of delay time

$$CR \leq t_d \leq C(R + R_W)$$

$$3.57ms \leq t_d \leq 18.97ms$$

2. What's the functionality of the resistor next to  $R_w$ ?

It prevents short circuit when  $R_w$  is set to 0.

- **Problem 3 - 9.8**

1. Analyse the status of Fig9.8 when S is open.

2.

3.

- **Problem 4 - 9.13**.

## Session 7 - Sequential circuit and unit

---

### Session 2 Homework

- **Problem 1 - 10.2**.

- **Problem 2 - 10.6**.

- **Problem 3 - 11.3**.

- **Problem 4 - 11.12**.