

Digital Circuit Fall 2019

Yuxuan Zhang, XJTU, 2160909016

Session 1 - Logical caculation and Binary code

Session 1 Notes

Logical Caculation

Basic logical operations:

NAME	OPERATOR	Example	Description
<i>AND</i>	\times	$A B$	All inputs are true
<i>OR</i>	$+$	$A + B$	One or more inputs are true
<i>NOT</i>	$\bar{}$	\bar{A}	Reverse input
<i>XOR</i>	\oplus	$A \oplus B$	One and only one input is true

Important tricks:

$$\overline{AB} = \bar{A} + \bar{B} \quad (1)$$

$$\overline{A + B} = \bar{A} \bar{B} \quad (2)$$

$$A + \bar{A}B = A + B \quad (3)$$

$$A + AB = A \quad (4)$$

Session 1 Homework

- **Problem 1 - 2.3 (3)** Convert 145.6875_D to Binary.

For integer part:

$$145_D = 1001\ 0001_B$$

For decimal part:

$$0.6875_D = 0.1011_B$$

Hence:

$$145.6875_D = 1001\ 0001.1011_B$$

- **Problem 2 - 2.7 (4)** Prove Logical Equation: $BC + AD = (B + A)(B + D)(A + C)(C + D)$.

Proof:

LHS:

$$\begin{aligned} AB + CD &= \overline{\overline{AB + CD}} \\ &= \overline{\overline{BC} \overline{AD}} \\ &= \overline{(\bar{B} + \bar{C})(\bar{A} + \bar{D})} \\ &= \overline{\bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C} + \bar{C}\bar{D}} \end{aligned}$$

RHS:

$$\begin{aligned}
 (B + A)(B + D)(A + C)(C + D) &= \overline{\overline{(B + A)(B + D)(A + C)(C + D)}} \\
 &= \overline{\overline{(B + A)} + \overline{(B + D)} + \overline{(A + C)} + \overline{(C + D)}} \\
 &= \overline{\bar{A}\bar{B} + \bar{B}\bar{D} + \bar{A}\bar{C} + \bar{C}\bar{D}}
 \end{aligned}$$

Hence:

$$LHS = RHS$$

Prove Complete.

- **Problem 3 - 2.8 (4)** Find the Reverse Expression of Logical function $L_4 = (A + \bar{B})(\bar{A} + \bar{B} + C)$.

$$\begin{aligned}
 \overline{L_4} &= \overline{(A + \bar{B})(\bar{A} + \bar{B} + C)} \\
 &= \overline{(A + \bar{B})} + \overline{(\bar{A} + \bar{B} + C)} \\
 &= \bar{A}B + \overline{(\bar{A} + \bar{B})}\bar{C} \\
 &= \bar{A}B + ABC \\
 &= \bar{A}B + BC
 \end{aligned}$$

- **Problem 4 - 2.11** Consider a specific Logical Circuit with three input A, B and C , its output is 1 when ture inputs are more than false inputs, vice versa. Draw value chart of this circuit and find its Logic Expression.

A	B	C	Output
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1
0	0	1	0
1	0	1	1

$$L = AB + BC + AC$$

- **Problem 5 - 2.13 (7)** Simplify Logical Function: $L = \overline{(AB + \bar{B}C)(AC + \bar{A}\bar{C})}$.

$$\begin{aligned}
L &= \overline{(AB + \bar{B}C)(AC + \bar{A}\bar{C})} \\
&= \overline{(AB + \bar{B}C)} + \overline{(AC + \bar{A}\bar{C})} \\
&= \bar{A}\bar{B}\bar{B}\bar{C} + \bar{A}\bar{C}\bar{A}\bar{C} \\
&= (\bar{A} + \bar{B})(B + \bar{C}) + (\bar{A} + \bar{C})(A + C) \\
&= \bar{A}B + \bar{A}\bar{C} + \bar{B}B + \bar{B}\bar{C} + \bar{A}A + \bar{A}C + \bar{C}A + \bar{C}C \\
&= \bar{A}(\bar{C} + C) + \bar{A}B + \bar{B}\bar{C} + \bar{C}A \\
&= \bar{A} + \bar{B}\bar{C} + \bar{C}A \\
&= \bar{A} + \bar{B}\bar{C} + \bar{C} \\
&= \bar{A} + \bar{C}
\end{aligned}$$

- **Problem 6 - 2.15 (6)** Use Carno Chart to simplify $L = \Sigma m(2, 3, 4, 5, 9) + \Sigma d(10, 11, 12, 13)$.

$CD \backslash AB$	00	01	11	10
00			1	1
01	1	1		
11	x	x		
10		1	x	x

$$L = \bar{A}D + A\bar{D} + BC\bar{D}$$

Session 2 - Digital circuit architecture

Session 2 Homework


- **Problem 1 - 3.11** Analyze logic circuit.

Truth Table:

A	0	1
L	1	1

$$L = \text{True}$$

Wave Form ($t_{pd} = 50ns$):

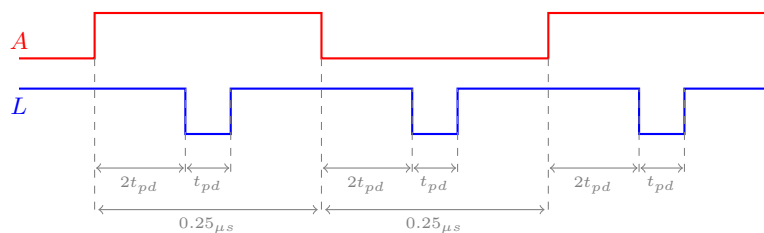

• **Problem 2 - 3.15 (c)** Analyze logic circuit.

At the case of $X \rightarrow HIGH$:

$$L = Z$$

At the case of $X \rightarrow LOW$:

$$L = A\bar{B}$$

• **Problem 3 - 3.16** Pull or Push.

应该选用 (a) 方案, 因为 74 系列 TTL 可以接受的灌电流 ($I_{OL} = 16mA$) 远大于高电平时的极限输出电流 ($I_{OH} = -0.4mA$), 更适合驱动负载。且在本例中, 考虑到 $I_{LED} = 10mA$, 只有 I_{OL} 满足此条件。

• **Problem 4 - 3.20** Multyfunctional gate array.

(1) Give the expression of Y (no simplification required):

$$Y = \overline{E_3 A B + E_2 \bar{A} B + E_1 A \bar{B} + E_0 \bar{A} \bar{B}}$$

(2) Give the functionality of this circuit with $E_3 E_2 E_1 E_0 \rightarrow 0000 - 0111$:

E	$functionality$		
0 0 0 0	$Y =$	$True$	
0 0 0 1	$Y =$	$\bar{A}\bar{B}$	$= A + B$
0 0 1 0	$Y =$	$\bar{A}B$	$= \bar{A} + B$
0 1 0 0	$Y =$	$\bar{A}\bar{B}$	$= A + \bar{B}$
0 0 1 1	$Y =$	$\bar{A}\bar{B} + \bar{A}B$	$= B$
0 1 0 1	$Y =$	$\bar{A}B + \bar{A}\bar{B}$	$= A$
0 1 1 0	$Y =$	$\bar{A}B + A\bar{B}$	$= AB + \bar{A}\bar{B}$
0 1 1 1	$Y =$	$\bar{A}B + A\bar{B} + \bar{A}\bar{B}$	$= AB$

(2) Caculate the value range of R according to given conditions:

First of all, we should be aware that there are AT MOST 2 Gates at LOW status. While ALL four gates may be at HIGH status.

In case of 3 Highs and 1 Low, we get:

$$\begin{cases} 5V - R \cdot I_{CC} < 0.3V \\ I_{CC} + 0.4mA \times 2 + 100\mu A \times 3 < 8mA \end{cases}$$

In case of 4 Highs, we get:

$$\begin{cases} 5V - R \cdot I_{CC} > 3V \\ I_{CC} + 100\mu A \times 4 > 20\mu A \times 2 \end{cases}$$

Hence:

$$R > 681\Omega$$

Session 3

Session 3 Homework

• **Problem 1 - 4.12** Analyze waveform.

ANALYSIS:


At the down-edge of CLK1, Q1 ALWAYS flips itself;

When $Q_1 = 1$, at the down-edge of CLK2, Q2 flips itself;

When $Q_1 = 0$, at the down-edge of CLK_2 , Q_2 is set to 0;

When $Q_2 = 1$, Q_1 is IMMEDIATELY reset to 0;

Hence:

 

• Problem 2 - 5.4 Analyze logic relations.


ANALYSIS:

$J_1 \equiv K_1 \equiv 1$, hence Q_1 is flipped at each down-edge of CP

$J_2 \equiv K_2 = \bar{X} Q_1 + X \bar{Q}_1 \equiv X \oplus Q_1$

$Y = \bar{X} Q_1 Q_2 + X \bar{Q}_1 \bar{Q}_2$

WAVEFORM:

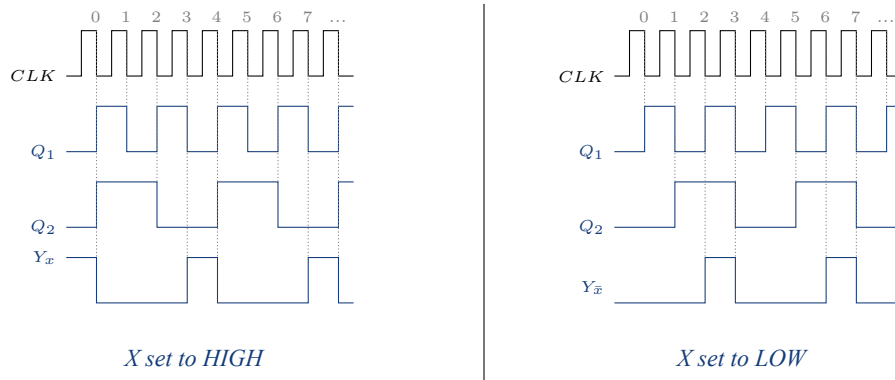

CONCLUSION:

无论当 $X = LOW$ 或 $X = HIGH$, Y 端均生成一个占空比为 25%, 频率为四分之一 CLK 频率的方波. X 的高低仅改变波的相位.

Session 4 - Digital circuit architecture

Session 4 Homework

• Problem 1 - 7.6 Analyze Specific 74LS153 Functionality.

Truth Table (1ST Enabled):


$CD \setminus AB$	00	01	11	10	Functionality
00	1	1	0	1	$not(A \text{ and } B)$
01	1	0	0	0	$not(A \text{ or } B)$
11	0	0	0	0	$False$
10	1	0	1	0	$not(A \text{ xor } B)$

$$L = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + \bar{A}\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} + ABC\bar{D}$$


When 1ST is Disabled:

$$L = Z$$

 • **Problem 2 - 7.7** Logic circuit design.




• **Problem 3 - 7.8** Logic circuit design.

 


Session 5 - Sequential circuit and unit

Session 5 Notes

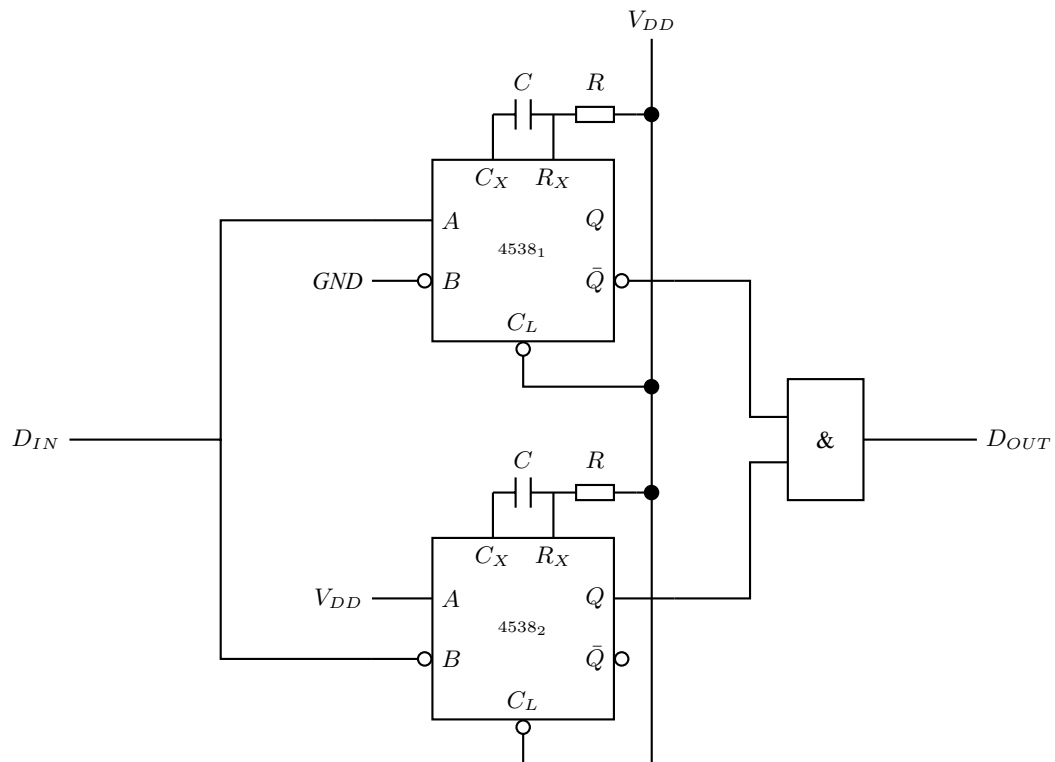Another method to generate delayed pulse - without losing its length




Functionality analysis:

 

Session 5 Homework

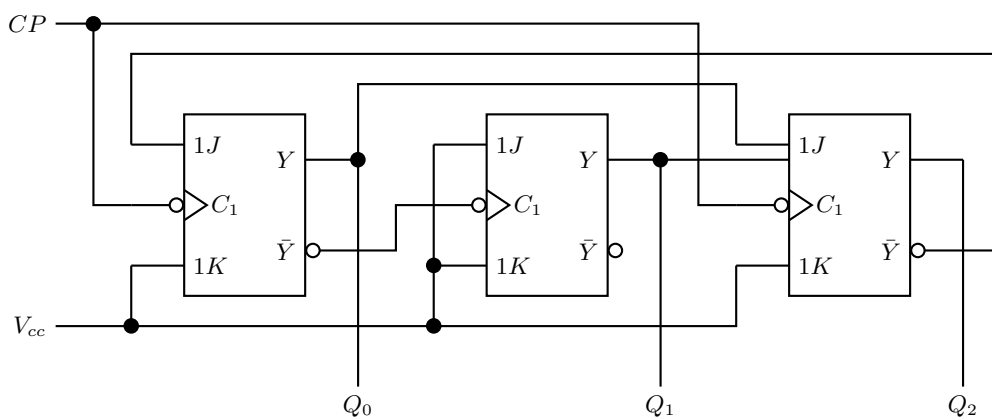
- **Problem 1 - 8.3** Analyze Logical function of the given circuit.




$K \equiv 1, J=1$ flip, $J=0$ reset.

CP	Q_0	Q_1	Q_2	Q_0^N	Q_1^N	Q_2^N	CP^N
0	0	0	0	1	1	0	6
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	4
3	0	1	1	0	1	0	2
4	1	0	0	0	0	0	0
5	1	0	1	0	0	0	0
6	1	1	0	0	1	1	3
7	1	1	1	0	1	0	2


Carno Chart:

 

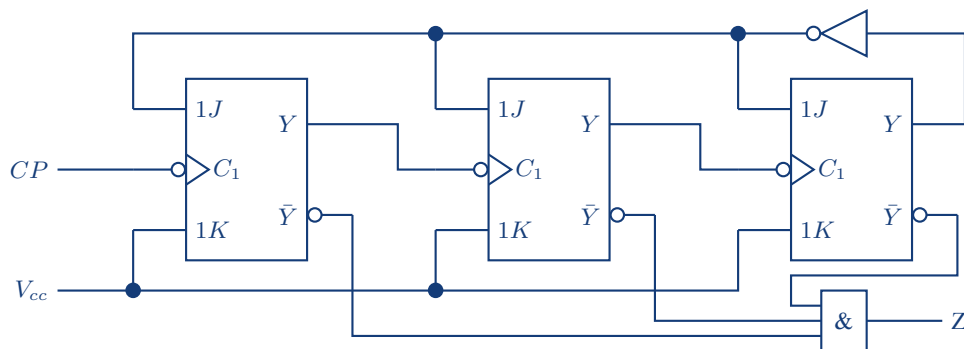- **Problem 2 - 8.6** Design a circuit using Jump-Key flip-flop to serve given function.



 - **Problem 3 - 8.7** Build a 60 counter with 74LS293.



- **Problem 4 - 8.12** Analyze Logical function of the given circuit.

The given circuit forms a **196 counter** with initial value **60** and ending value **255**.

- **Problem 5 - 8.13** Give the value saved in each register according to given waveform.

CP	Reg_1	Reg_2	Reg_3	Action(s)
t_0	1011	1000	0111	Chip Initialized
t_1	1011	1000	1000	MOV R3,R2
t_2	1011	1000	1000	Enable R3 (No ST)
t_3	1011	1000	1000	No action
t_4	1011	1011	1011	MOV {R2,R3},R1

- **Problem 6 - 8.17** Given design of logical circuit:

1. List state sequence of the circuit, with initial state 0110

CP	Q_0	Q_1	Q_2	Q_3	Note
0	0	1	1	0	Initial
1	0	0	1	1	→
2	1	0	0	1	→
3	1	1	0	0	→
4	0	1	1	0	Repeat CP_0


2. List the output sequence of L

CP	Q_0	Q_1	Q_2	Q_3	$D_{Selected}$	Y
0	0	1	1	0	D_3	0
1	0	0	1	1	D_1	1
2	1	0	0	1	D_4	0
3	1	1	0	0	D_6	0

Session 6 - Pulse generating and shaping

Session 6 Homework

 - **Problem 1 - 9.1** Give the waveform of u_0 .



- **Problem 2 - 9.5** Given a 74121 connected as shown.

1. Calculate the range of delay time

$$CR \leq t_d \leq C(R + R_w)$$

$$3.57ms \leq t_d \leq 18.97ms$$

2. What's the functionality of the resistor next to R_w ?

It prevents short circuit when R_w is set to 0.

• Problem 3 - 9.8

1. Analyze the status of circuit when S is open.

When S remains open,

$$\overline{TR} \equiv V_{cc} > \frac{1}{3} V_{cc}$$

TH will be flipped to Low if it was High, and remains Low as a stable status.

Hence, u_0 holds on 0. The circuit is stable.

2. Let $C = 10 \mu F$, give the value of R so as the circuit outputs a pulse of $t_w = 10s$ when S is pressed.

Since the given design is a standard monostable trigger, we can use $t_w = RC \ln 3 = 10s$.

Hence, $R = 910 k\Omega$.

3. What's the value of R if $C = 0.1 \mu F$, $t_w = 5 ms$? What value of t_w do we expect if we replace C by $1 \mu F$ with the same R ?

$$t_w = RC \ln 3 = 5 ms$$

$$R = \frac{5 ms}{0.1 \mu F \cdot \ln 3} = 45.5 k\Omega$$

$$\text{Replace} \Rightarrow C = 1 \mu F$$

$$t_w = 50 ms$$

• Problem 4 - 9.13 .

1. What kind of function dose each of the 555 chip serve?

Each of them is a multivibrator.

2. Analyze the status of circuit when S is set to 1.

Charging time:

$$(\text{Chip1}) T_1 = (R_1 + R_2)C \ln 2 = 2.84 ms$$

$$(\text{Chip2}) T_1 = (R_1 + R_2)C \ln 2 = 0.284 ms$$

Discharge time:

$$(\text{Chip1}) T_2 = R_2 C \ln 2 = 1.53 ms$$

$$(\text{Chip2}) T_2 = R_2 C \ln 2 = 0.153 ms$$


Duty cycle:

$$(\text{Chip1}) F = 228.3 Hz$$

$$(\text{Chip2}) F = 2.283 kHz$$

Ratio 65%


3. Draw the waveform of both u_0 and u_1 when S is set to 2.

 

Session 7 - Memory, D/A and A/D Converter

Session 7 Homework

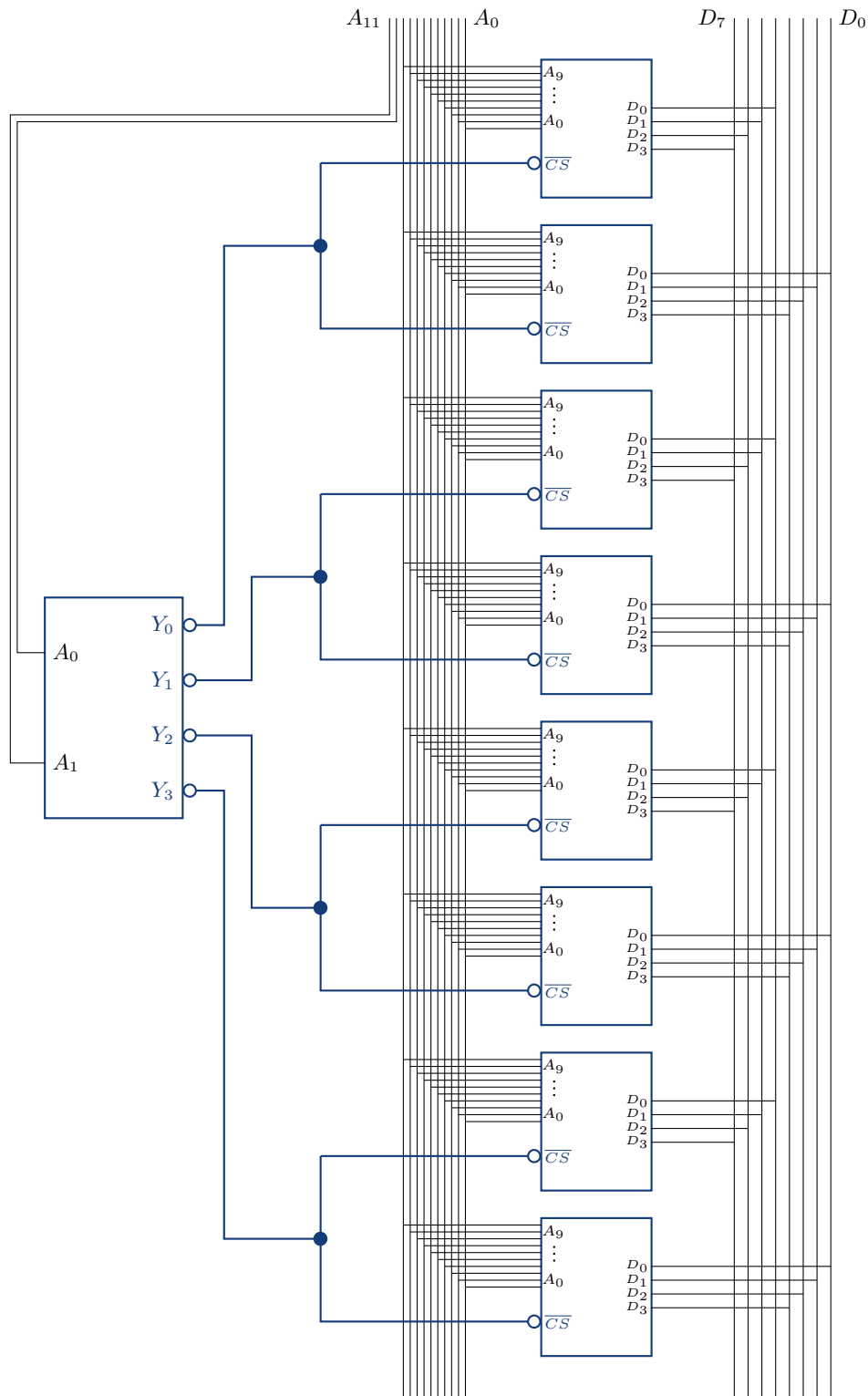- **Problem 1 - 10.2** Build a RAM of 4096 Byte with 8 pieces of 1024*4b RAM and a 2-4 decoder.



- **Problem 2 - 10.6** Analyze simple memory system.

One of the memory chip works when:

$$M/\bar{IO} = 1$$


$$WR = 1 \text{ or } RD = 1$$

(And, of course) when address is valid

The valid addresses are:

$$0x00000 \sim 0x00FFF$$

• **Problem 3 - 11.3 Circuit Design.**

 

• **Problem 4 - 11.12 ADC circuit design principles.**

Levels of measurement:

$$2^N \geq \frac{400}{0.1}$$

$$N_{min} = 12$$

Maximun converting time:

$$T_{max} = \frac{1s}{32} = 31.25ms$$